


EXPERIMENT-4.

PUSH BUTTON SWITCH INTERFACE-DOOR BELL CONTROL

AIM-Design a door bell using push button.

***APPARATUS-Arduino,Resistance 470
ohm,wires,breadboard,push button***

CIRCUIT DIAGRAM:

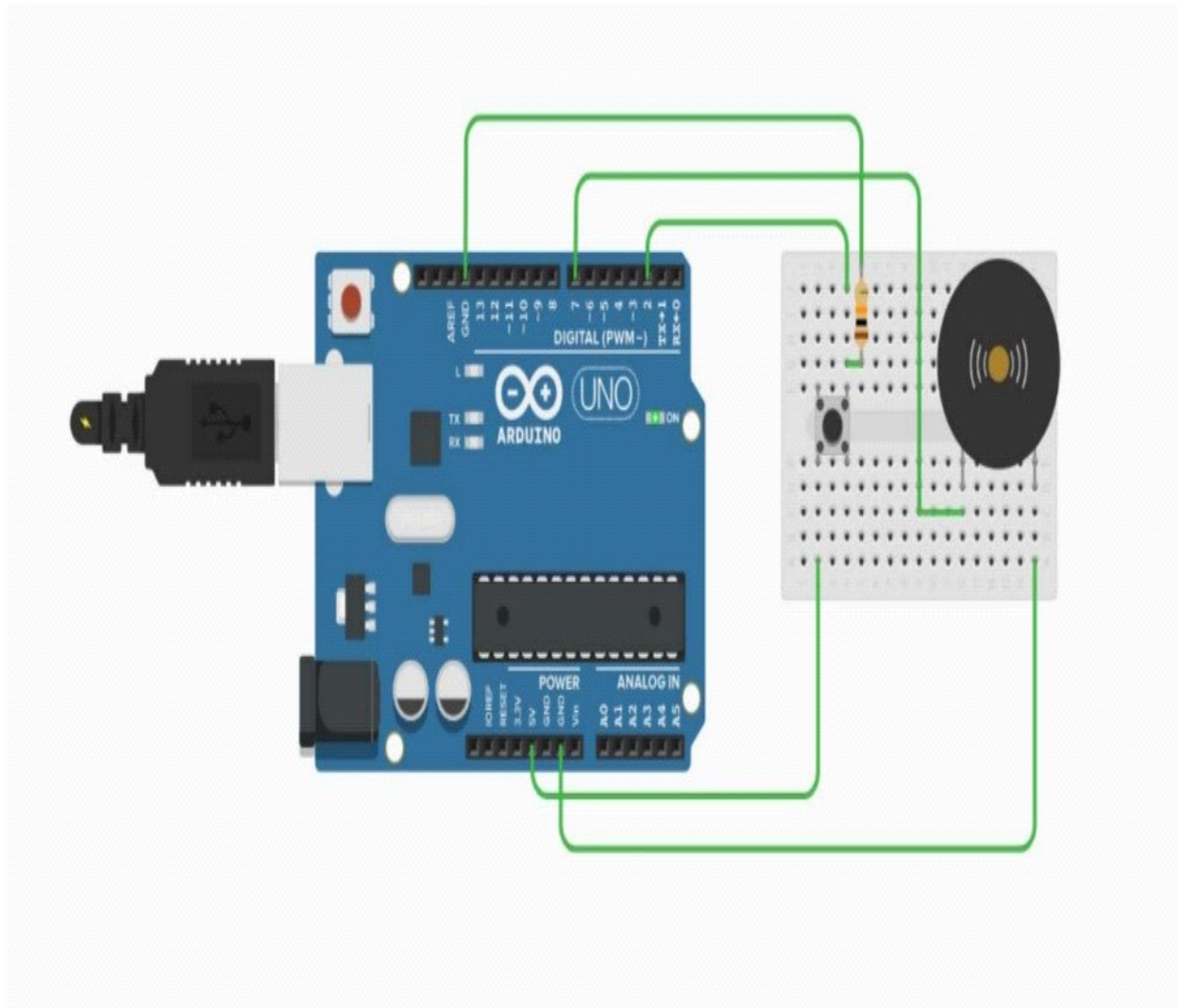

THEORY

CONCEPT USED:-

- *We have used pushbutton as a switch*
- *Each time you press the button, the bell will start making noise.*

Learning and observation:-

- *I have learned how we can use switch to operate different devices.*

Problem and troubleshooting:

- *Port selection should be done properly where you have connected arduino to the system .*
- *connections were loose.*
- *switch was not working.*

Precautions:

- *Make sure the connections are proper.*
- *Select the appropriate port.*

- *Make sure the connections are not loose.*

Learning outcome:

- *I learned how we can use a simple switch to make a door bell.*
- *I also gained some basic knowledge of arduino.*